

ECE 110 - Exam Jam

Stewart Aitchison

Preparing for the exam

- Develop a study plan or timetable
- Decide which topics you need to spend most time on
- Review Wiley Plus examples, and midterm papers
- Look at old exam papers

The Final Exam

- The Final Assessment will cover all materials listed in the course syllabus.
- The Final Assessment questions will be taken from the WileyPlus question pool and administered on WileyPlus (similar to the Assignments and Term Test-1 and Term Test-2)
- There will be 7 questions on the Final Assessment, and students will receive similar questions
 - One question on electrostatics
 - Two questions on magnetism
 - Two questions on DC circuit analysis
 - One question on the first-order transient circuit
 - One question on AC circuit analysis

Calculators

- FASE approved Calculators are:
 - Casio fx-991 MS and
 - Sharp EL-520X
- Make sure you know how to use them
 - Simultaneous Equations (2x2) and (3x3)
 - Physical constants - ϵ_0 and μ_0
 - Complex numbers – addition, subtraction, multiplication and division, polar – rectangular conversion
- Can you solve:
 - $(4k + 6k)I_1 - 6kI_3 = -6$
 - $(9k + 3k)I_2 - 3kI_3 = 6$
 - $-6kI_1 - 3kI_2 + (3k + 6k + 12k)I_3 = 0$
- And
 - $I = \frac{V}{Z} = \frac{12\sqrt{2}\angle 90^\circ}{4\sqrt{2}\angle 45^\circ}$


Topics covered in ECE 110

- Electrostatics, Gauss's Law, electric potential, Capacitors and Resistors
- Magnetic Fields, and Ampere's Law and Faraday's Law, Inductors
- DC circuits
- First Order Circuits
- AC Circuits

Gauss' Law

- Relates the electric flux through a closed surface to the charge enclosed by that surface.
- Key Ideas:
 - $\Phi = \oint \vec{E} \cdot d\vec{A}$ *o-*
 - Both \vec{E} and $d\vec{A}$ are vectors.

Gauss' Law

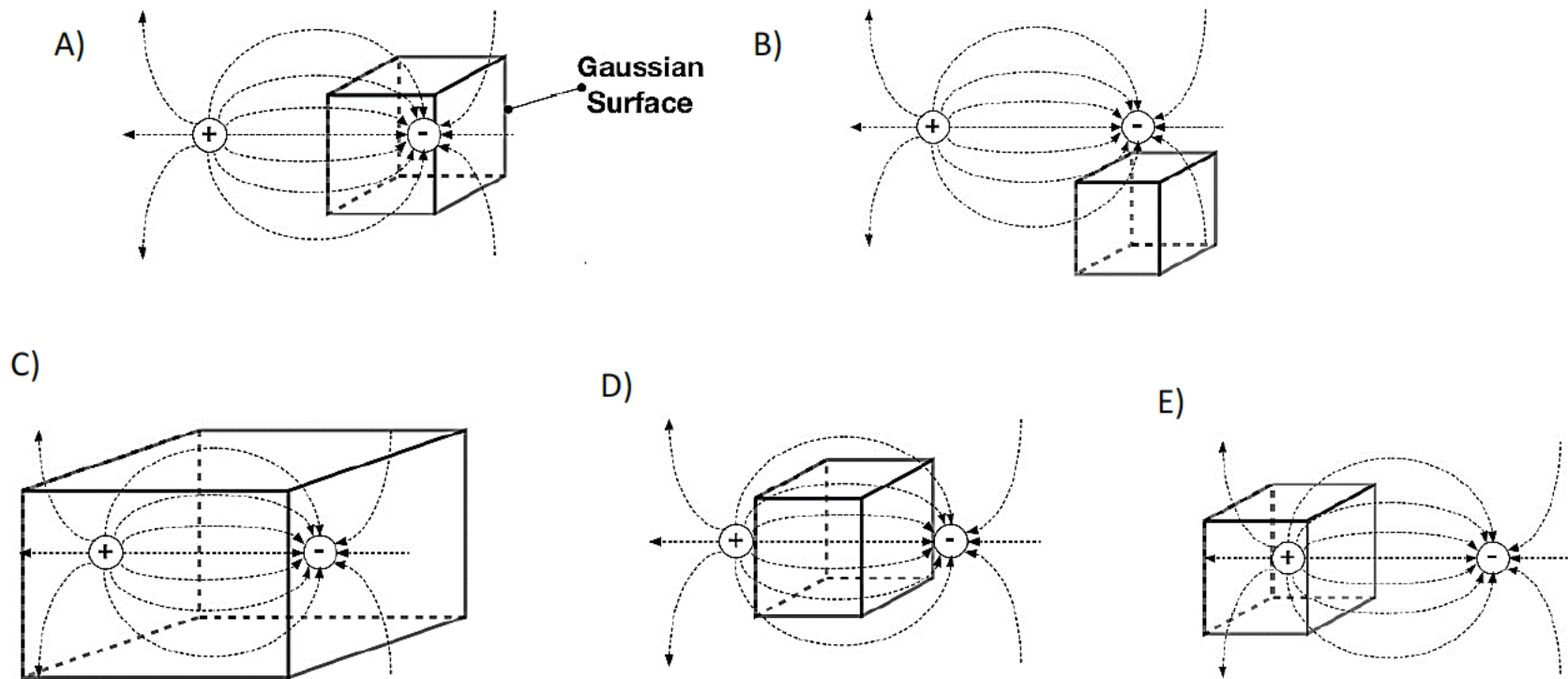

Biot Savart Law

The magnitude of the field $d\mathbf{B}$ produced at point P at distance r by a current-length element $d\mathbf{s}$ turns out to be

$$d\mathbf{B} = \frac{\mu_0}{4\pi} \frac{i ds \sin \theta}{r^2},$$


where θ is the angle between the directions of $d\mathbf{s}$ and $\hat{\mathbf{r}}$, a unit vector that points from $d\mathbf{s}$ toward P. Symbol μ_0 is a constant, called the permeability constant, whose value is defined to be exactly

$$\mu_0 = 4\pi \times 10^{-7} \text{ T}\cdot\text{m/A} \approx 1.26 \times 10^{-6} \text{ T}\cdot\text{m/A}.$$


The direction of $d\mathbf{B}$, shown as being into the page in the figure, is that of the cross product $d\mathbf{s} \times \hat{\mathbf{r}}$. We can therefore write the above equation containing $d\mathbf{B}$ in vector form as

$$d\vec{\mathbf{B}} = \frac{\mu_0}{4\pi} \frac{i d\vec{\mathbf{s}} \times \hat{\mathbf{r}}}{r^2}$$

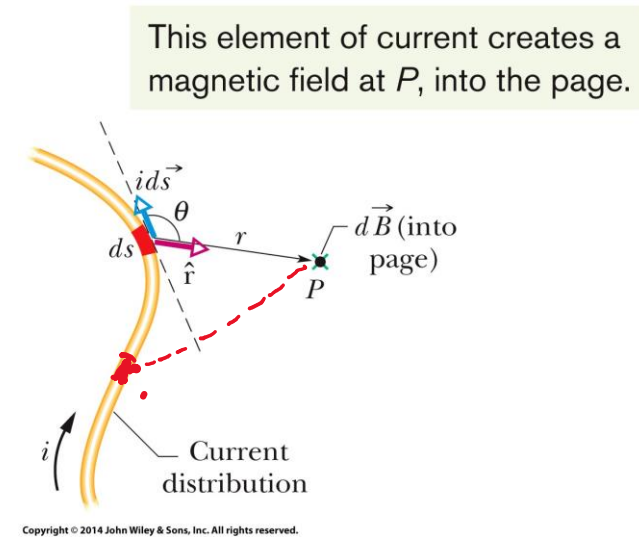This vector equation and its scalar form are known as the **law of Biot and Savart**.



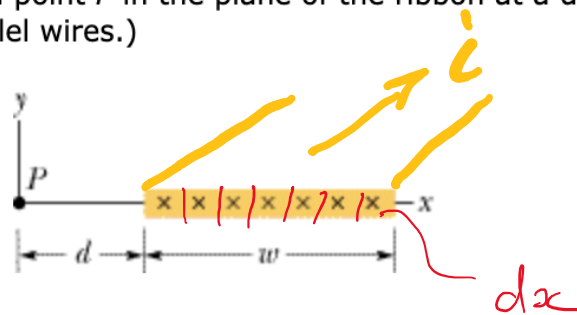The figure below shows a cross section of a long thin ribbon of width $w = 4.75$ cm that is carrying a uniformly distributed total current $i = 6.47$ μ A into the page. Calculate the magnitude of the magnetic field at a point P in the plane of the ribbon at a distance $d = 2.04$ cm from its edge. (Hint: Imagine the ribbon as being constructed from many long, thin, parallel wires.)



Think.

$$B = \frac{\mu_0 i}{2\pi r}$$

Solve

$$di = i \frac{dx}{w}$$

$$dB = \frac{\mu_0 di}{2\pi x} = \frac{\mu_0 i dx}{2\pi w x}$$

$$B = \int dB = \frac{\mu_0 i}{2\pi w} \int_d^{d+w} \frac{dx}{x}$$

$$B = \frac{\mu_0 i}{2\pi w} \ln\left(1 + \frac{w}{d}\right)$$

check.

$$d \gg w$$

$$\ln(1+x) = x - \frac{x^2}{2} \dots$$

$$\rightarrow B_P \rightarrow \frac{\mu_0 i}{2\pi d}$$

Ampere's Law

- Can be expressed as: $\oint \vec{B} \cdot d\vec{s} = \mu_0 i_{enc}$
- i_{enc} is the current enclosed by the Amperian Loop
- Q: Inside a long metallic conductor, carrying a current I , where is the magnetic field $B = 0$
 - A. At the center
 - B. At the surface
 - C. Outside
 - D. Everywhere inside the conductor.



Ampere's Law

Ampere's law states that

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 i_{enc}$$

The line integral in this equation is evaluated around a closed loop called an Amperian loop. The current i on the right side is the net current encircled by the loop.



Curl your right hand around the Amperian loop, with the fingers pointing in the direction of integration. A current through the loop in the general direction of your outstretched thumb is assigned a plus sign, and a current generally in the opposite direction is assigned a minus sign.


Magnetic Fields of a long straight wire with current:

$$B = \frac{\mu_0 i}{2\pi r} \quad (\text{outside straight wire}).$$

$$B = \left(\frac{\mu_0 i}{2\pi R^2} \right) r \quad (\text{inside straight wire}).$$

© 2014 John Wiley & Sons, Inc. All rights reserved.

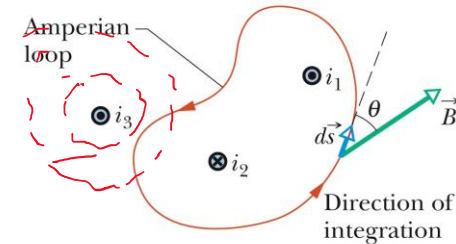
Only the currents encircled by the loop are used in Ampere's law.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Ampere's law applied to an arbitrary Amperian loop that encircles two long straight wires but excludes a third wire. Note the directions of the currents.

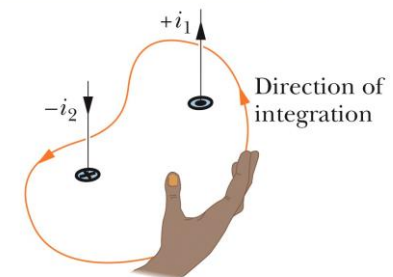
This is how to assign a sign to a current used in Ampere's law.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Magnetic Fields due to currents

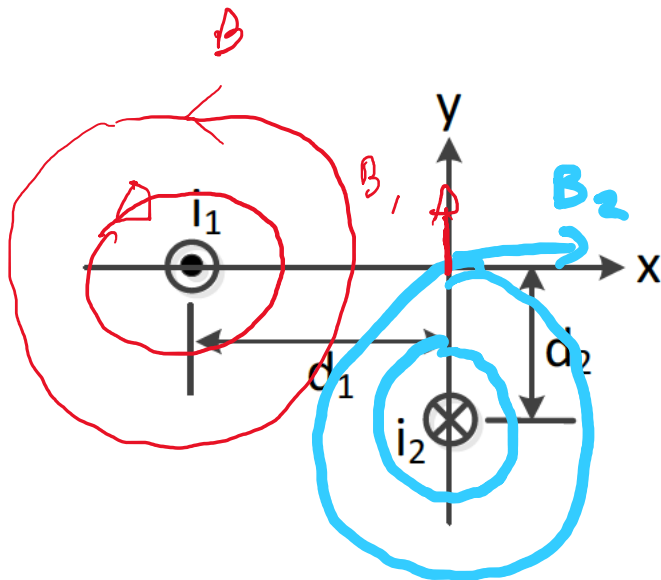- For two long straight wires as shown, which expression describes the magnetic field at the origin?



~~i) $\frac{\mu_0 i_2}{2\pi d_2} \hat{i}$~~

~~ii) $\frac{\mu_0 i_1}{2\pi d_1} \hat{j}$~~


~~iii) $\frac{\mu_0 i_2}{2\pi d_2} \hat{i} - \frac{\mu_0 i_1}{2\pi d_1} \hat{j}$~~

~~iv) $\frac{\mu_0 i_1}{2\pi d_2} \hat{i} + \frac{\mu_0 i_2}{2\pi d_1} \hat{j}$~~

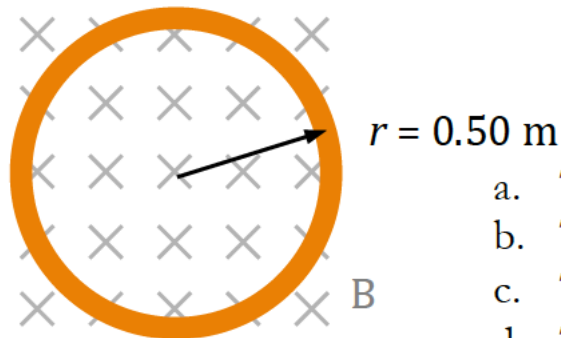v) $\frac{\mu_0 i_2}{2\pi d_2} \hat{i} + \frac{\mu_0 i_1}{2\pi d_1} \hat{j}$ ✓

Faraday's Law


- $\underline{\mathcal{E}} = -\frac{d\Phi_B}{dt}$ where the flux is given by: $\Phi_B = \int \vec{B} \cdot d\vec{A} = B \int dA = \underline{B\pi r^2}$
- The flux induced always opposes the change in the flux of B. However, B induced is not always opposite to B.
- Consider the loop in a constant B field with $B = 4 \text{ T}$, which statement is true:



- The flux through the loop is 0, and current flows in the counterclockwise direction.
- The flux through the loop is 0, and current flows in the clockwise direction.
- The flux through the loop is π Webers, and current flows in the clockwise direction.
- The flux through the loop is π Webers, and current flows in the counterclockwise direction.
- ✓ The flux through the loop is π Webers, and the current is 0. ✓

Faraday's Law

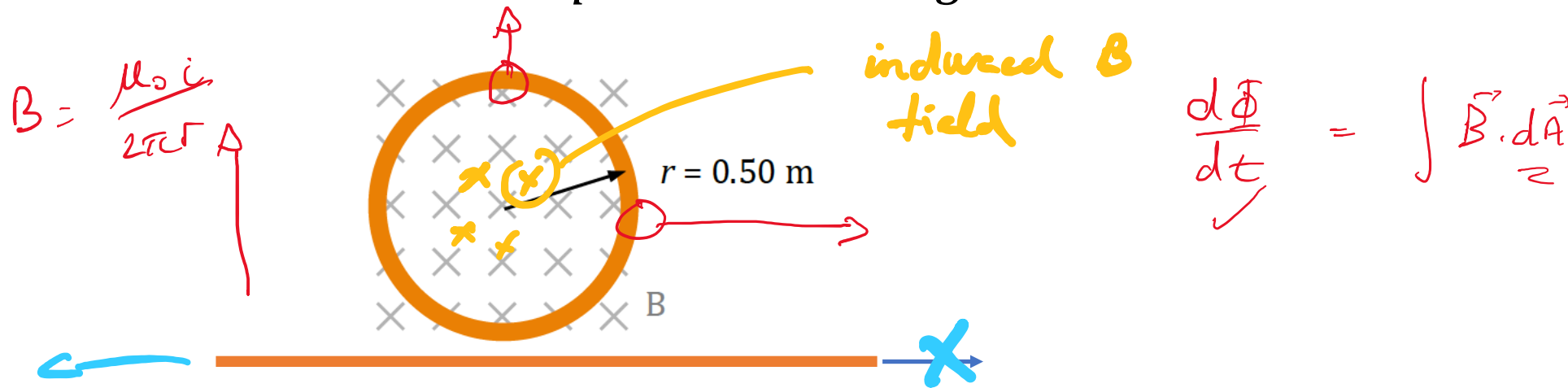- Now consider the loop next to a long wire:




- What is the direction of the current in the loop if it is moving parallel to the wire?
- What is the direction of the current in the loop if it is moving away from the wire?

DC circuits - Concept Questions


- The circuit has two identical light bulbs connected to a battery. What happens to the brightness of A and B when the switch is closed?

$$P = iV$$

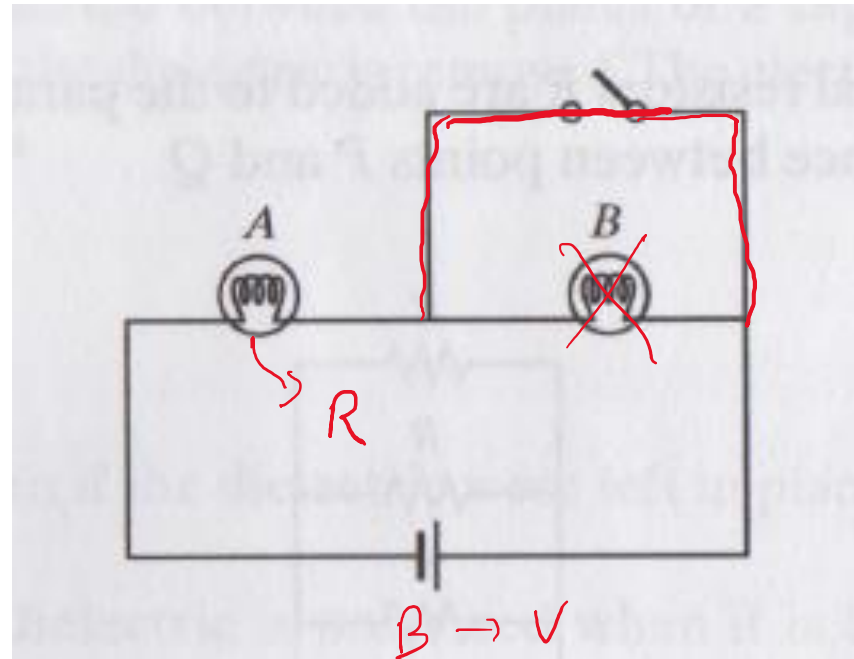

Concept Questions


- Which circuit generates more light?

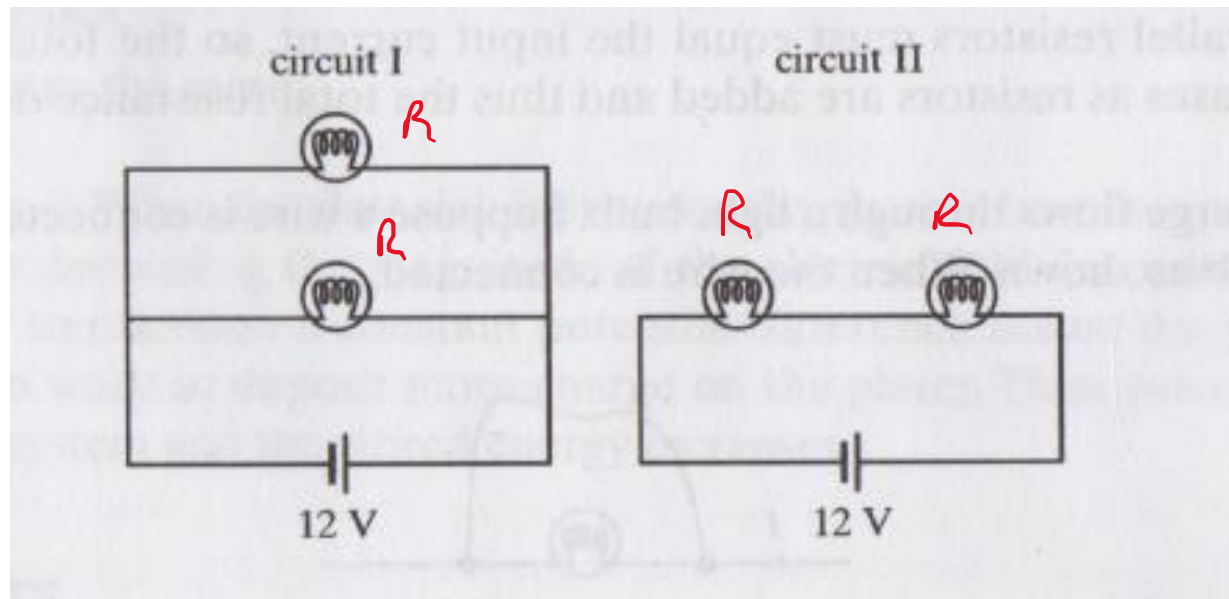

DC Circuits

Q3 [10 marks]

Consider the following circuit:

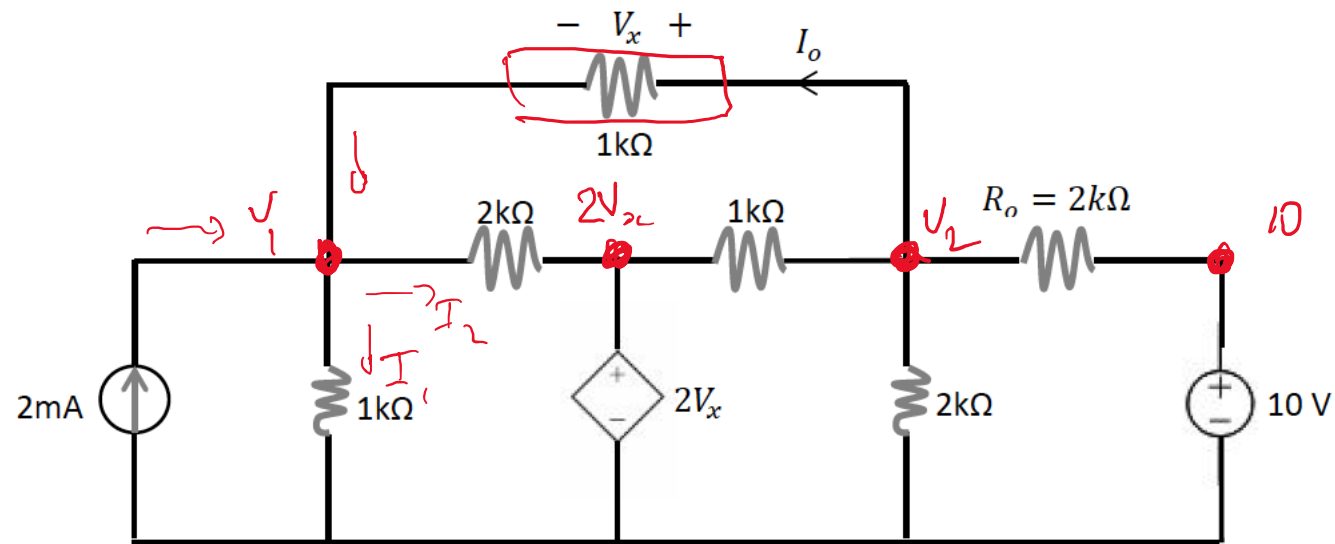

1) Think


2) solve

3) check

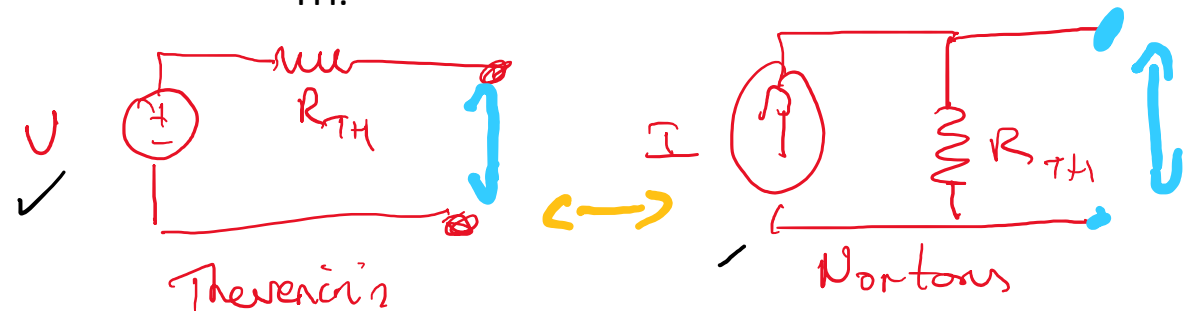(a) [7 marks] Compute I_o using Nodal Analysis


Thévenin's and Norton's

- Remove the load and find the open circuit voltage of the circuit
- To determine the R_{TH} depends on the circuit
 - Only independent sources. Replace voltage sources with short circuits and current sources with open circuits
 - Only Dependent sources. Connect an independent current or voltage source to the terminals and calculate the voltage or current. Use Ohm's Law to calculate R_{RH}
 - Both Dependent and Independent sources. Short circuit the output terminals and calculate i_{sc} . Use this with v_{oc} to calculate R_{TH} .
- For Norton's start with i_{sc}



First order circuits

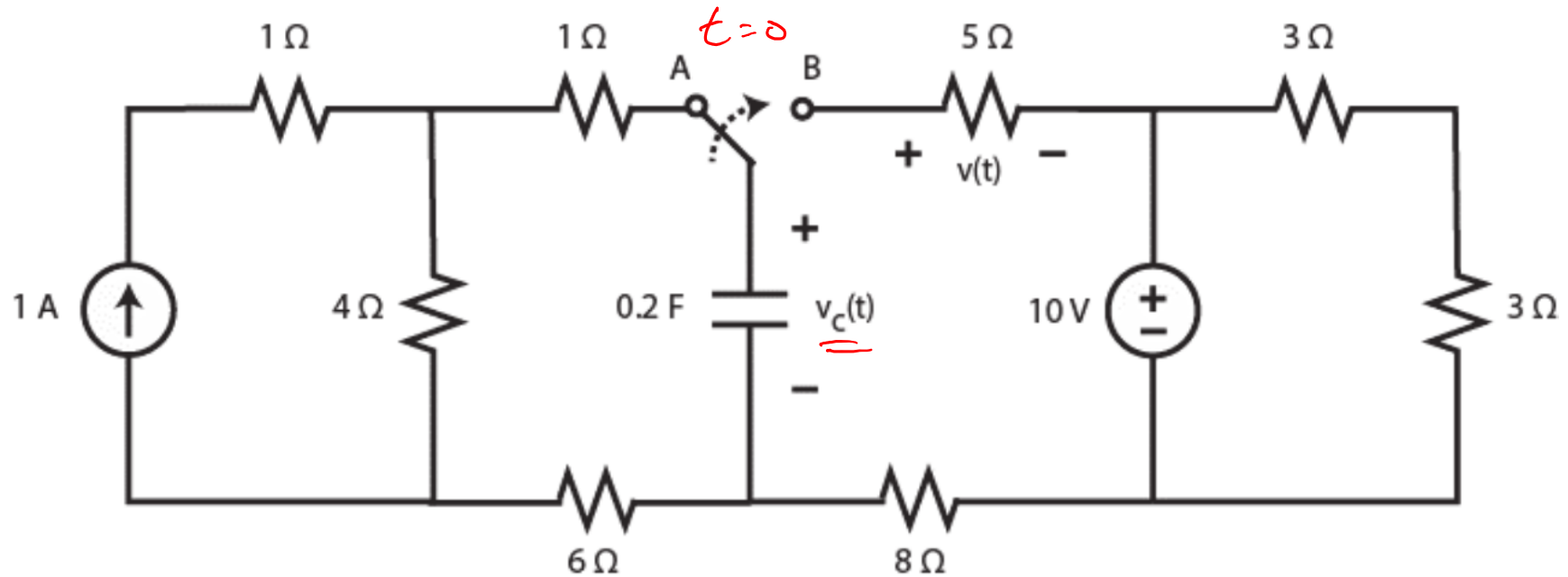- Can you find an expression for $v_c(t)$ and $v(t)$ for $t > 0$




First order circuits

- Have a solution of the form: $v(t)$ or $i(t) = K_1 + K_2 e^{-\frac{t}{\tau}}$ ←
- Time constant $\tau = RC$ or L/R .
- K_1 is the steady state solution. →
- K_2 is the transient solution at $t=0$ we know $e^0 = 1$
- The current through an inductor is a continuous function
 - $i_l(t = 0^-) = i_l(t = 0^+)$ ← → Faraday Law
- The voltage across a capacitor is a continuous function
 - $v_c(t = 0^-) = v_c(t = 0^+)$ ← → charging a capacitor

First order circuits

A capacitor in a DC circuit
is an open circuit

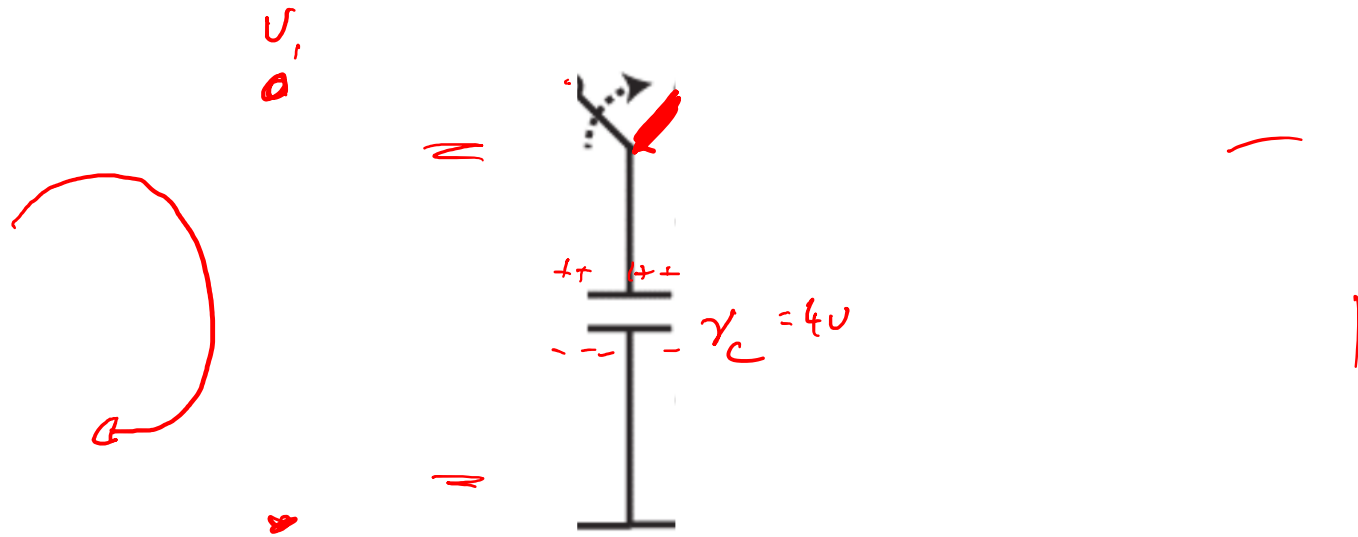- Can you find an expression for $v_c(t)$ and $v(t)$ for $t > 0$




$$U = iR = 5$$

$$V_4 = 5 \left(\frac{4}{1+4} \right) = 4V = U_c$$

LEARNING EXAMPLE

FIND THE OUTPUT VOLTAGE $v_o(t); t > 0$

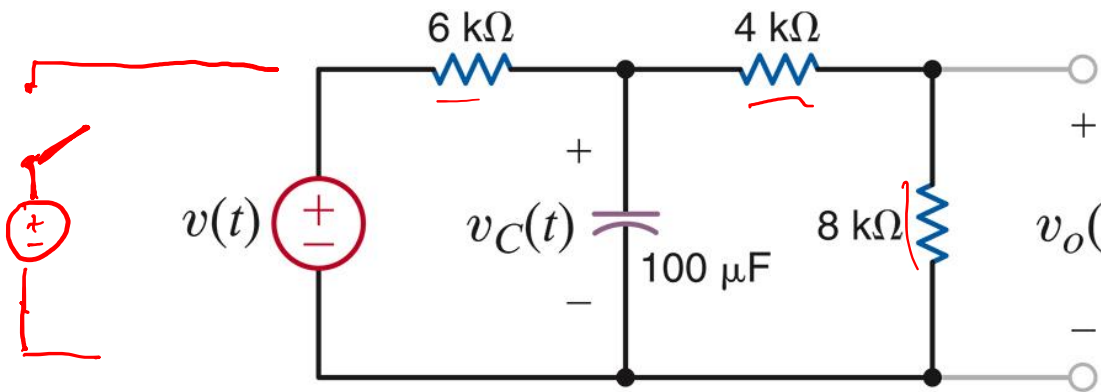

$t > 0.3 \Rightarrow v(t) = 0 \quad t_o = 0.3$



$v_o(0.3+) = 4(1 - e^{-\frac{0.3}{0.4}})$

$v_o(t) = K_1'' + K_2'' e^{-\frac{(t-0.3)}{\tau'}}$

$\tau' = 0.4$

$v_o(\infty) = 0 \Rightarrow K_1'' = 0$

$K_2'' = v_o(0.3+) = 2.11(V)$

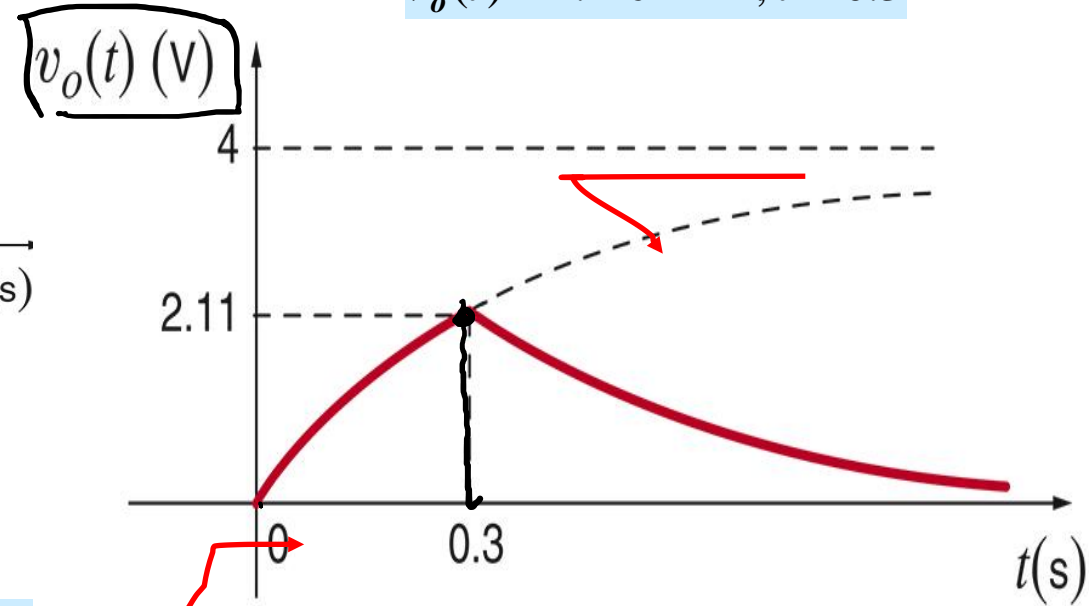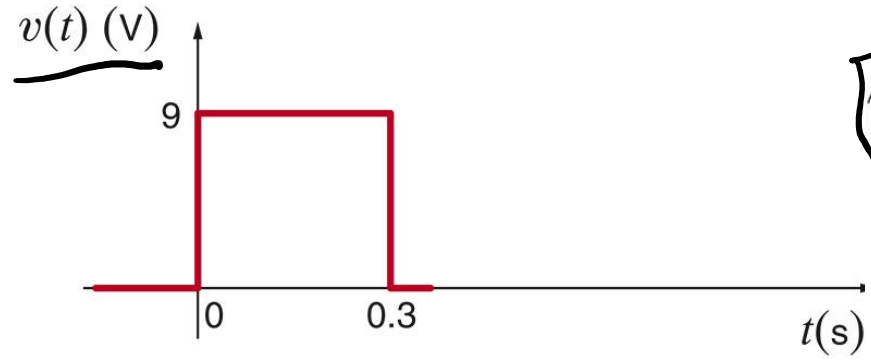

$v_o(t) = 2.11 e^{-\frac{t-0.3}{0.4}} ; t > 0.3$

$t \leq 0 \Rightarrow v(t) = 0 \Rightarrow v_o(t) = 0 \quad v_o(0+) = 0$

$t \geq 0^+ \Rightarrow v(t) = 9V$

$v_o(t) = K_1' + K_2' e^{-\frac{t}{\tau}}$

$\tau = R_{TH}C = (6k \parallel 12k) \times 100\mu F = 0.4s$

$v_o(\infty) = \frac{8}{10+8}(9) = K_1'$

$v_o(0+) = K_1' + K_2' = 0$


$v_o(t) = 4 \left(1 - e^{-\frac{t}{0.4}} \right)$

AC circuits

- Express voltages, and currents as Phasors
 - $I = I_m \angle \Theta_I$ ←
 - $V = V_m \angle \Theta_v$ ←
- Impedance is a complex number which depends on ω
 - $Z = Z_m \angle \Theta_z = \underline{R} + jX(\omega)$
- For simple circuits use Ohm's law
- Apply KVL, KCL, superposition etc
- Thevenin's, Norton's etc

IMPEDANCE AND ADMITTANCE

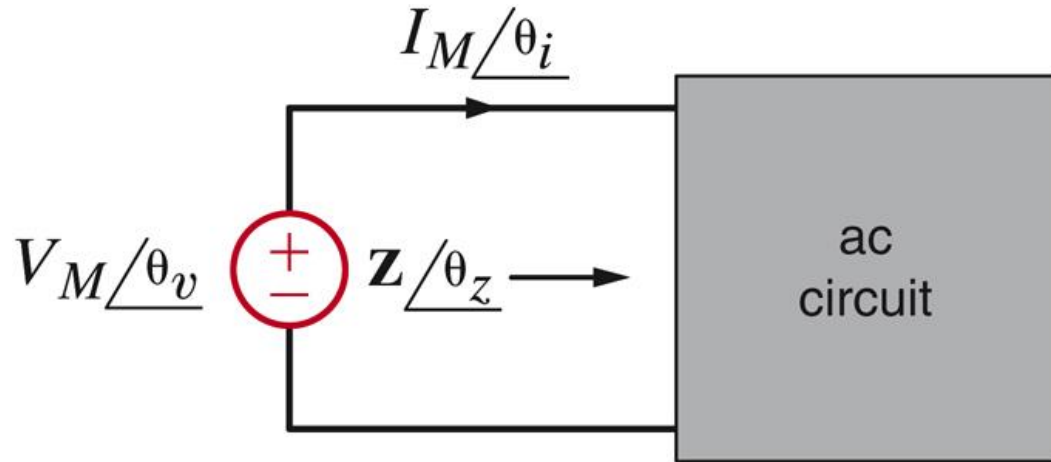For each of the passive components the relationship between the voltage phasor and the current phasor is algebraic. We now generalize for an arbitrary 2-terminal element.



$$\mathbf{Z}(\omega) = \mathbf{R}(\omega) + j\mathbf{X}(\omega)$$

$\mathbf{R}(\omega)$ = Resistive component

$\mathbf{X}(\omega)$ = Reactive component

$$|\mathbf{Z}| = \sqrt{\mathbf{R}^2 + \mathbf{X}^2}$$

$$\theta_z = \tan^{-1} \frac{\mathbf{X}}{\mathbf{R}}$$

(INPUT) IMPEDANCE

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{V_M \angle \theta_v}{I_M \angle \theta_i} = \frac{V_M}{I_M} \angle (\theta_v - \theta_i) = |\mathbf{Z}| \angle \theta_z$$


(DRIVING POINT IMPEDANCE)

The units of impedance are OHMS.

Impedance is NOT a phasor but a complex number that can be written in polar or Cartesian form. In general, its value depends on the frequency.

Element	Phasor Eq.	Impedance
R	$V = RI$	$Z = R$
L	$V = j\omega LI$	$Z = j\omega L$
C	$V = \frac{1}{j\omega C} I$	$Z = \frac{1}{j\omega C}$

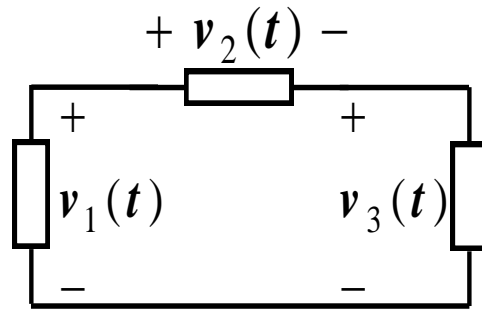KVL AND KCL HOLD FOR PHASOR REPRESENTATIONS





$$\text{KVL : } v_1(t) + v_2(t) + v_3(t) = 0$$

$$v_i(t) = V_{Mi} e^{j(\omega t + \theta_i)}, \quad i = 1, 2, 3$$

$$\text{KVL : } (V_{M1} e^{j\theta_1} + V_{M2} e^{j\theta_2} + V_{M3} e^{j\theta_3}) e^{j\omega t} = 0$$

$$V_{M1} \angle \theta_1 + V_{M2} \angle \theta_2 + V_{M3} \angle \theta_3 = 0$$

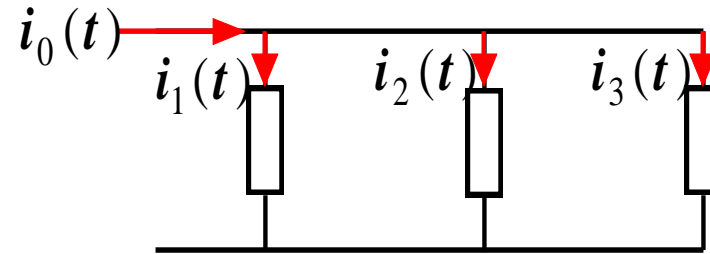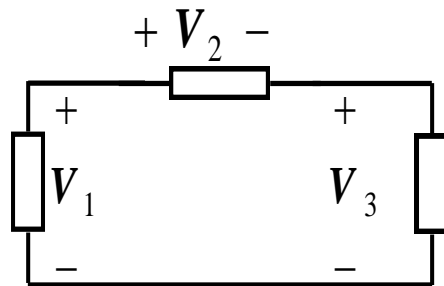
$$V_1 + V_2 + V_3 = 0 \quad \text{Phasors!}$$



$$\text{KCL : } -i_0(t) + i_1(t) + i_2(t) + i_3(t) = 0$$

$$i_k(t) = I_{Mk} e^{j(\omega t + \phi_k)}, \quad k = 0, 1, 2, 3$$



In a similar way, one shows ...

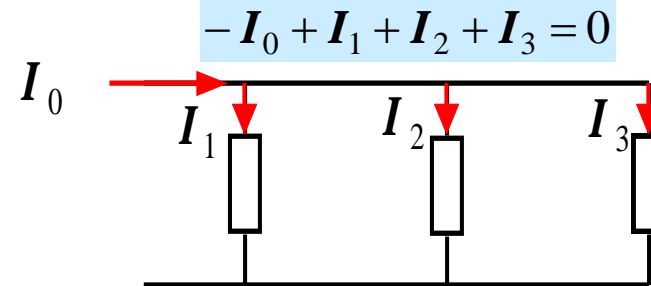


The components will be represented by their impedances and the relationships will be entirely algebraic!!



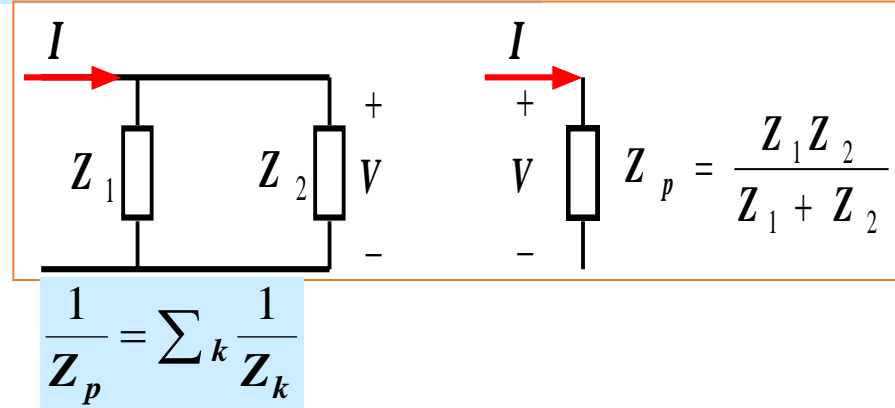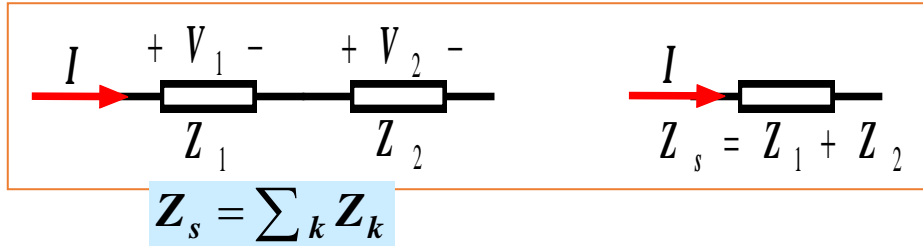SPECIAL APPLICATION:
 IMPEDANCES CAN BE COMBINED USING THE SAME RULES DEVELOPED
 FOR RESISTORS



LEARNING EXAMPLE

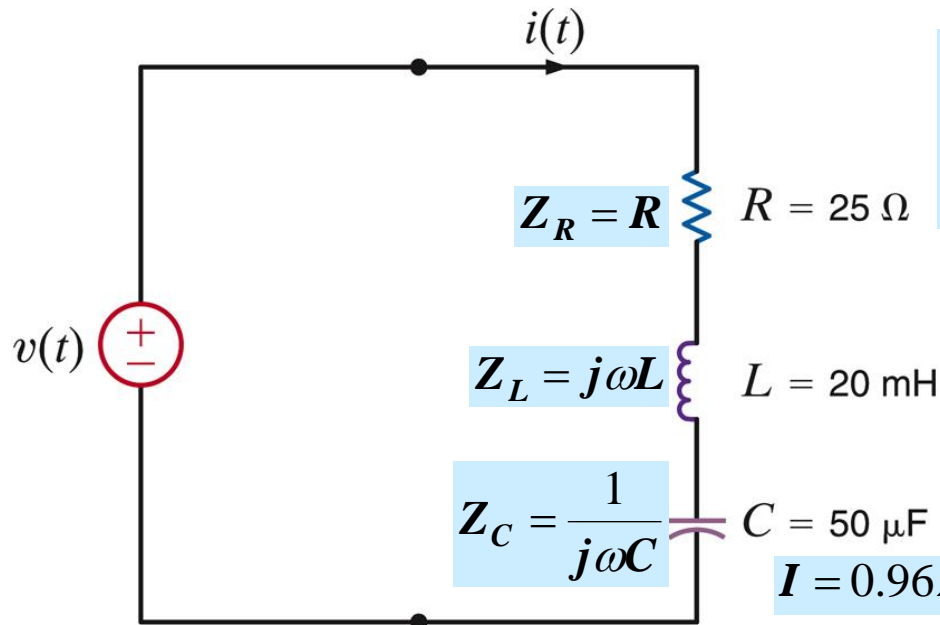

$f = 60\text{Hz}, v(t) = 50\cos(\omega t + 30^\circ)$
 Compute equivalent impedance and current
 $\omega = 120\pi, V = 50\angle 30^\circ, Z_R = 25\Omega$

$$Z_L = j120\pi \times 20 \times 10^{-3} \Omega, Z_C = \frac{1}{j120\pi \times 50 \times 10^{-6}}$$

$$Z_L = j7.54\Omega, Z_C = -j53.05\Omega$$

$$Z_s = Z_R + Z_L + Z_C = 25 - j45.51\Omega$$

$$I = \frac{V}{Z_s} = \frac{50\angle 30^\circ}{25 - j45.51} (\text{A}) = \frac{50\angle 30^\circ}{51.93\angle -61.22^\circ} (\text{A})$$


$$I = 0.96\angle 91.22^\circ (\text{A}) \Rightarrow i(t) = 0.96\cos(120\pi t + 91.22^\circ) (\text{A})$$



An AC circuit to consider

- At which frequencies does the light bulb glow brightest?

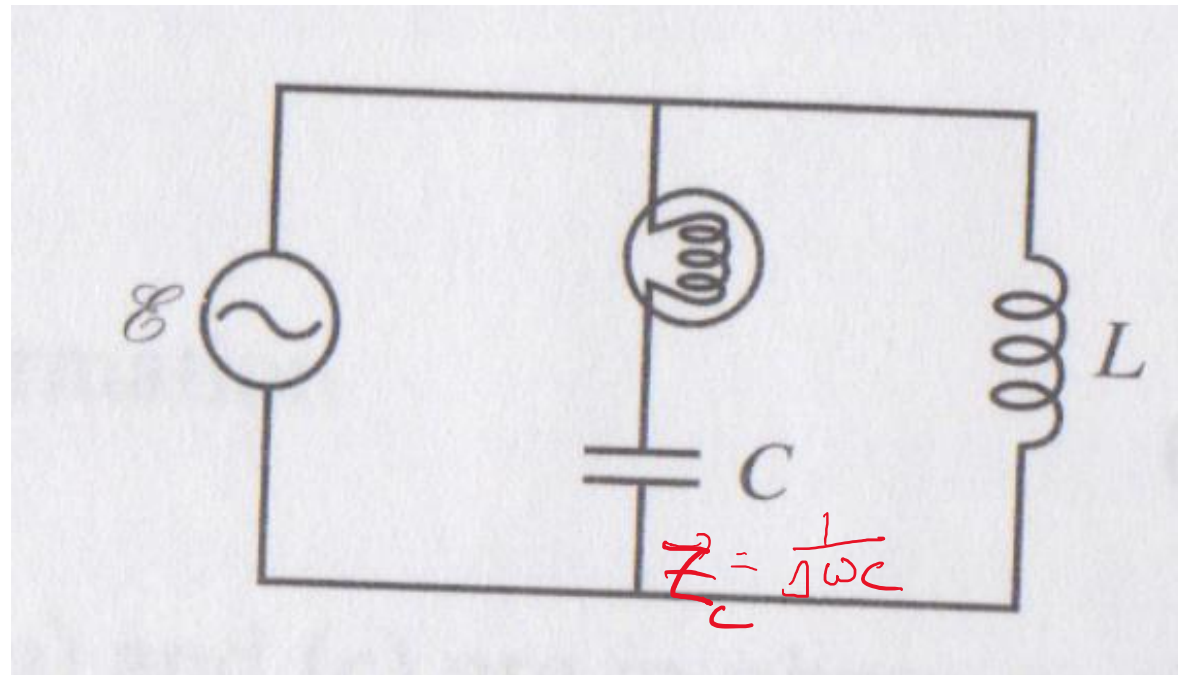- Low Frequencies
- High Frequencies ✓
- At $\omega = \frac{1}{\sqrt{LC}}$




$$\underline{Z_L = j\omega L}$$

ANALYSIS TECHNIQUES

PURPOSE: TO REVIEW ALL CIRCUIT ANALYSIS TOOLS DEVELOPED FOR RESISTIVE CIRCUITS; I.E., NODE AND LOOP ANALYSIS, SOURCE SUPERPOSITION, SOURCE TRANSFORMATION, THEVENIN'S AND NORTON'S THEOREMS.

COMPUTE I_0

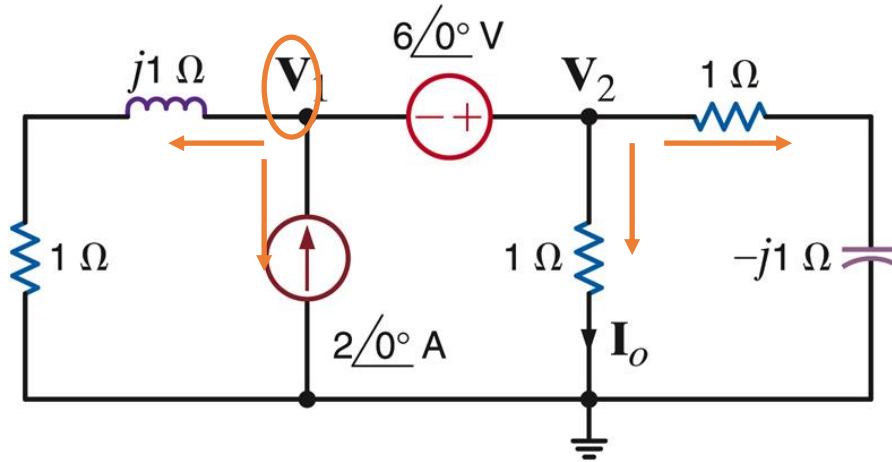

1. NODE ANALYSIS

$$\frac{V_1}{1+j1} - 2\angle 0^\circ + \frac{V_2}{1} + \frac{V_2}{1-j1} = 0$$

$$V_1 - V_2 = -6\angle 0^\circ$$

$$I_0 = \frac{V_2}{1} \text{ (A)}$$

$$\frac{V_2 - 6\angle 0^\circ}{1+j1} - 2\angle 0^\circ + V_2 + \frac{V_2}{1-j1} = 0$$

$$V_2 \left[\frac{1}{1+j1} + 1 + \frac{1}{1-j1} \right] = 2 + \frac{6}{1+j1}$$

$$V_2 \frac{(1-j1) + (1+j1)(1-j1) + (1+j1)}{(1+j1)(1-j1)} = \frac{2(1+j1) + 6}{1+j1}$$


$$V_2 \frac{4}{1-j} = 8 + j2$$

$$V_2 = \frac{(4+j)(1-j)}{2}$$

$$I_0 = \left(\frac{5}{2} - j\frac{3}{2} \right) \text{ (A)} \quad I_0 = 2.92 \angle -30.96^\circ$$

NEXT: LOOP ANALYSIS

2. LOOP ANALYSIS

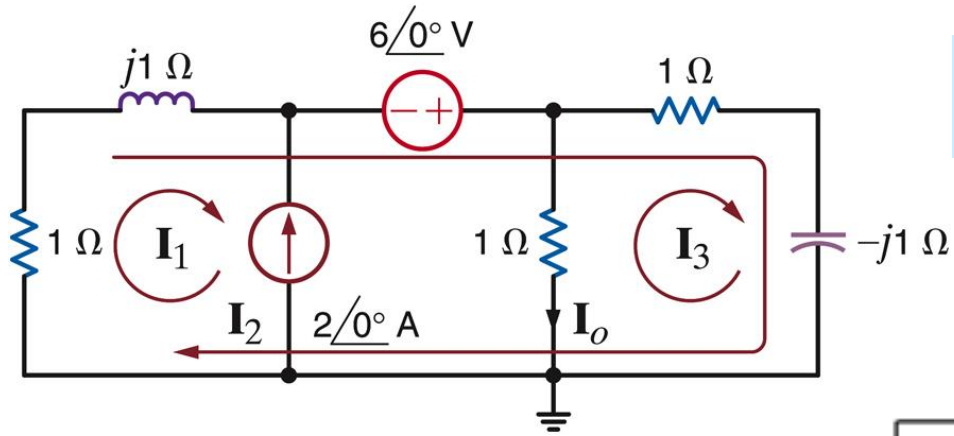

ONE COULD ALSO USE THE SUPERMESH TECHNIQUE

SOURCE IS NOT SHARED AND I_0 IS DEFINED BY ONE LOOP CURRENT

LOOP 1: $I_1 = -2\angle 0^\circ$

$I_0 = -I_3$

LOOP 2: $(1+j)(I_1 + I_2) - 6\angle 0^\circ + (1-j)(I_2 + I_3) = 0$

LOOP 3: $(1-j)(I_2 + I_3) + I_3 = 0$

MUST FIND I_3


$2I_2 + (1-j)I_3 = 6 - (1+j)(-2)$ $\left. \begin{array}{l} \text{ } \\ \text{ } \end{array} \right\} \begin{array}{l} /*(1-j) \\ /*(-2) \end{array}$

$(1-j)I_2 + (2-j)I_3 = 0$

$((1-j)^2 - 2(2-j))I_3 = (1-j)(8+2j)$

$I_3 = \frac{10-6j}{-4}$

$I_0 = \frac{5}{2} - \frac{3}{2}j(A)$

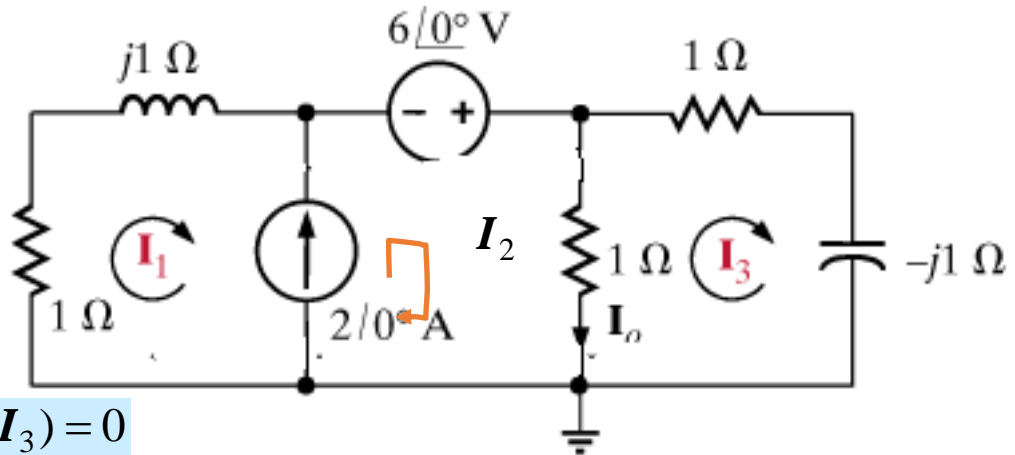

CONSTRAINT: $I_1 - I_2 = -2\angle 0^\circ$

SUPERMESH: $(1+j)I_1 + 6\angle 0^\circ + (I_2 - I_3) = 0$

MESH 3: $(I_3 - I_2) + (1-j)I_3 = 0$

$I_0 = I_2 - I_3$

